

6.002 Demo# 23


Demonstrates a resonant LC circuit Agarwal Fall 00

Lecture 15

Purpose:

This demonstrates the response of an LC circuit to a step, impulse, and sinusoid.

Steps:

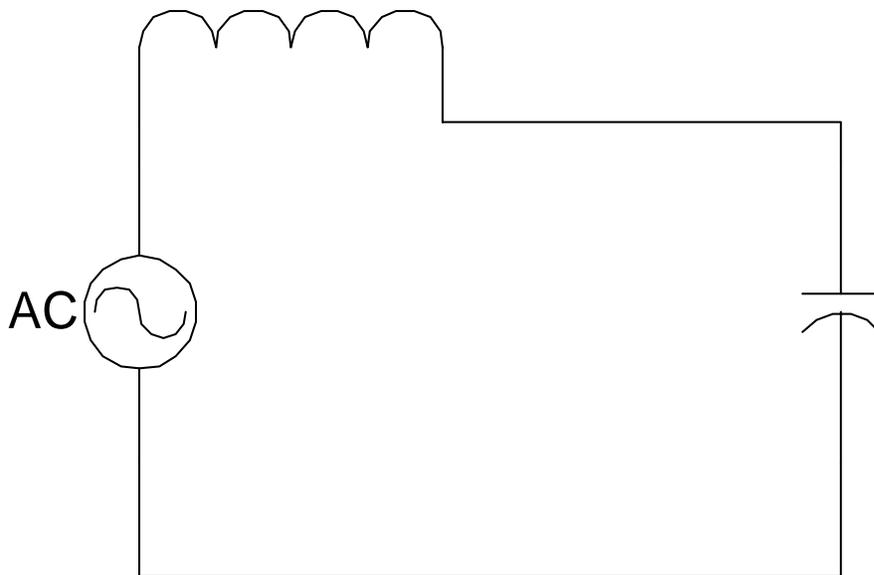

Part 1: Shows the response to a step.


Part 2: Shows the response to an impulse.

Part 3: Shows the response to sine wave manually swept through the resonance.

Series RLC For a long pulse load set up Demo#23L.set


Procedure:

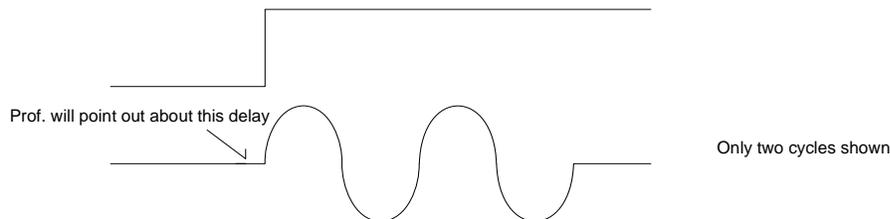- (1) For long pulse from IEC Gen. set the frequency at 4 HZ square wave
- Scope Sweep Skirt = 20 ms knob = .5 ms (Pull move to .5 ms then press it in)
- Single Sweep on
- Store on
- Ch1 = 2v/Div
- Ch2 = 2v/Div
- Time delay multiply ~645
- Use Diff Amp. to measure current Ch3 = 5v/Div, Ch4 = 5v/Div (current = .1v/Div)



For short pulse load set up Demo#23A.set

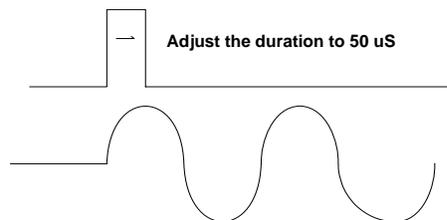- (2) For pulse generator (PG 501 ser # B010124) settings:
 - Period = 20 ms, Variable ~9.30
 - Duration = 10 microseconds, Variable ~ 11.30
 - Amplitude Max
 - Scope Ch2 = .5v/Div
 - Time delay multiply ~ 570
 - Ch3 = 5v/Div, Ch4 = .5v/Div (Current = 20 mV/Div)




If Prof. asks you about pulse width it is 50 microsecond, amplitude is 5 volts

Then he asks you to show the decaying signal just set scope sweep = 5 ms



Continues decreasing toward the ground

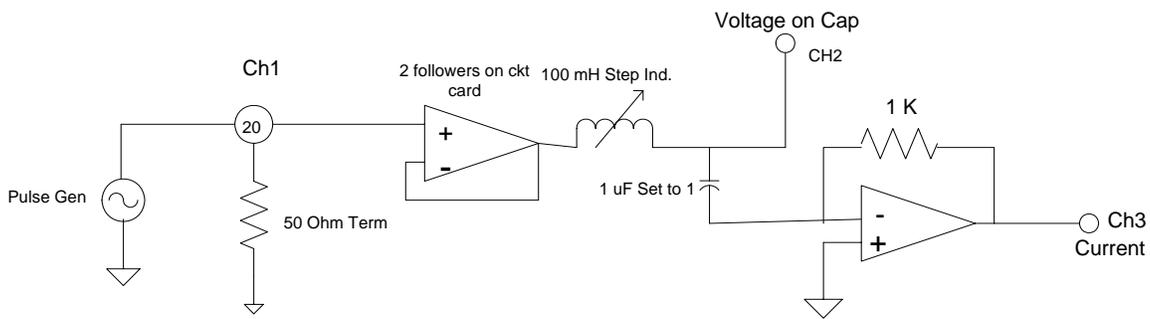- (3) Hand Sweep from IEC. Start from .3x1 Kh through resonance (Continuous Sinewave)
 - Gen . Amplitude at 3 v P-P Cal
 - Scope Sweep = .5 ms (Coupled skirt & knob together)
 - Ch1 = 5v/Div
 - Ch2 = 5v/Div



Do Not use 50 Ohm termination it's built on board!

NOTE: Set +/- 25 V supply at +/- 15 V for buffer

Do Pulse first and Second Lecture the Long Pulse with ICE generator